

**HPS experiment :
Current sensitive preamplifiers's
modifications
to fit the APD 10×10mm²**

Outline

- Physics : coupling between PbWO₄ crystals and APD 10×10mm²
- Previous preamplifier used for DVCS experiment (IC Calorimeter) with APD 5×5mm²
- Modification of the preamplifier N055 with APD 10×10mm²
- Conclusion
- Schedule




Physics : coupling between PbW04 crystals and $10\times 10\text{mm}^2$ APDs (1)

- HPS = 442 PbW04 crystals in truncated pyramidal shape.
 - Length = 160mm
 - Area at the front side (close to target) = $13\text{mm}\times 13\text{mm}$
 - Area at the back side (close to APD) = $16\text{mm}\times 16\text{mm}$
- Energy = from 10MeV up to 3GeV
- The coupling (number of photo-electrons/MeV) between the crystal and the APD is dependent of :
 - The quality of the crystal wrapping
 - The quality of the APD gluing
 - The quantum efficiency
 - The surface ratio between the crystal and APD (active area)

Physics : coupling between PbWO4 crystals and $10\times 10\text{mm}^2$ APDs (2)


- Estimate the theoretical number of photo-electrons/MeV
 - 120 photons/MeV in the PbWO4 crystal
 - Quantum efficiency = 70% for 420nm
 - Surface ration = 2.56 (= $(16\times 16)/(10\times 10)$)
- $\Rightarrow 35$ photo-electrons/MeV (= $120\times 0.75/2.56$)
- 4 times more than for $5\times 5\text{ mm}^2$ APD
- However , later , to take into account imperfections, we will use a pessimistic value = **25 photo-electrons/MeV**

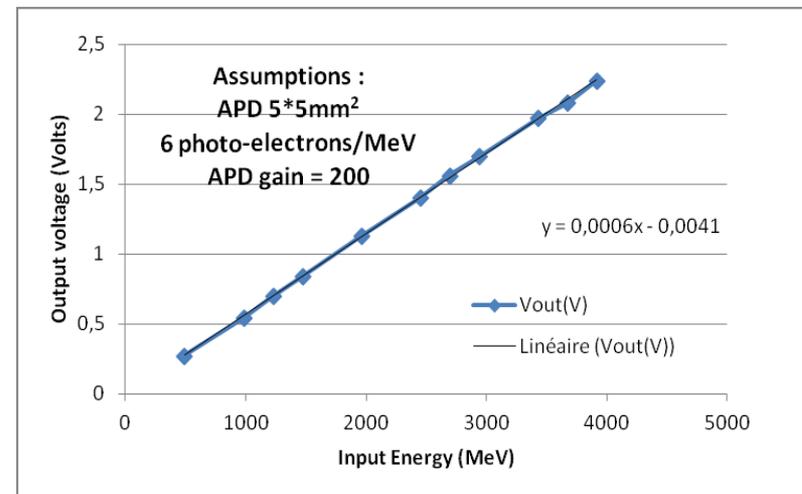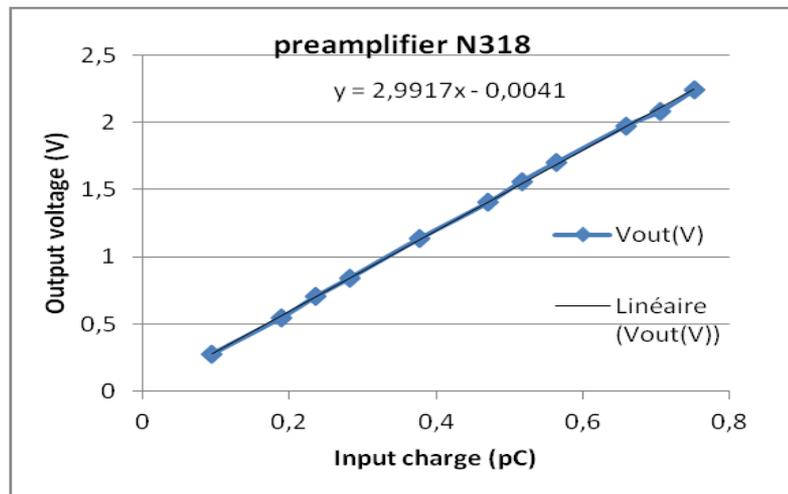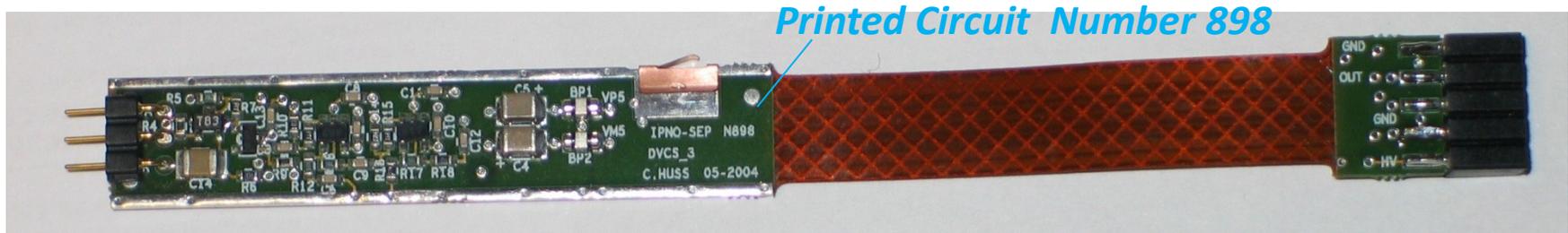Preamplifier used for DVCS IC calorimeter with $5 \times 5 \text{mm}^2$ APD (1)



Gain = **3V/pC** (Pulse Width = 20ns) or **0.6mV/MeV** (6 photo-electrons/MeV and APD gain = 200) or **2333 pC/pC** (=1.4nC/0.6pC)

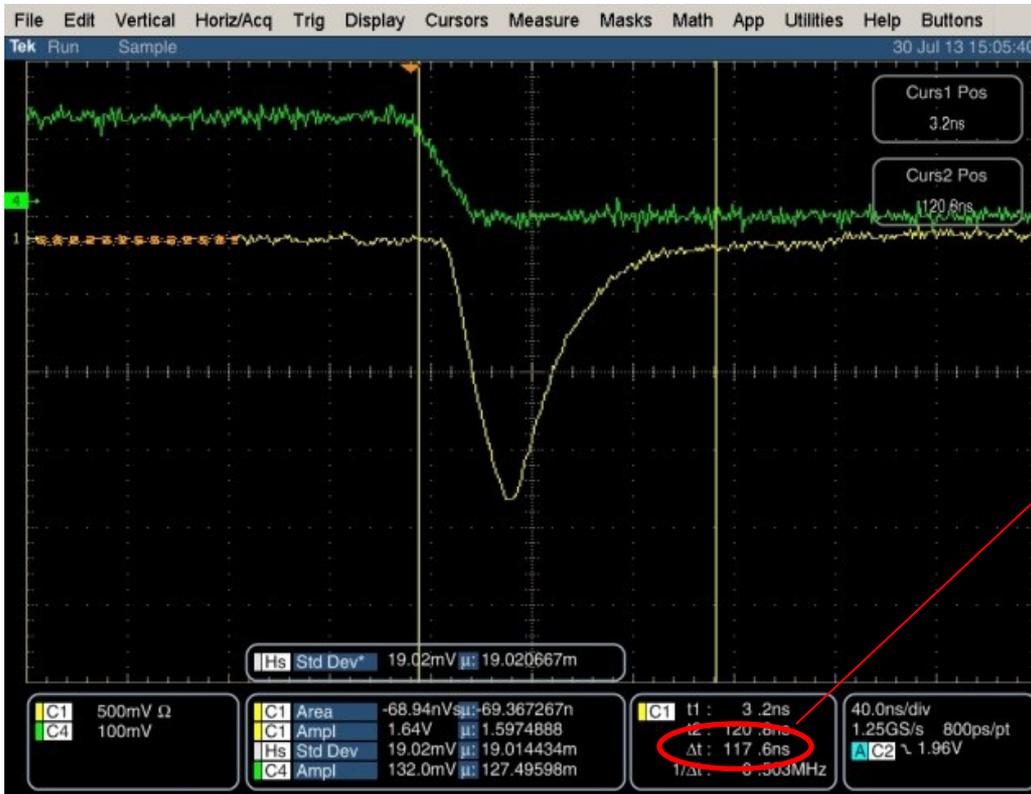Preamplifier used for DVCS IC calorimeter with $5 \times 5 \text{mm}^2$ APD (2)



- Output signal for $Q_{in}=0.6\text{pC}$ or $E_{in}=3\text{GeV}$ (PW=20ns, 6 photo-electrons/MeV and APD gain =200)


\Rightarrow Gate =120ns

\Rightarrow Amplitude = 1.6V

\Rightarrow Output charge = 1.4nC


\Rightarrow Input noise = 7.5MeV

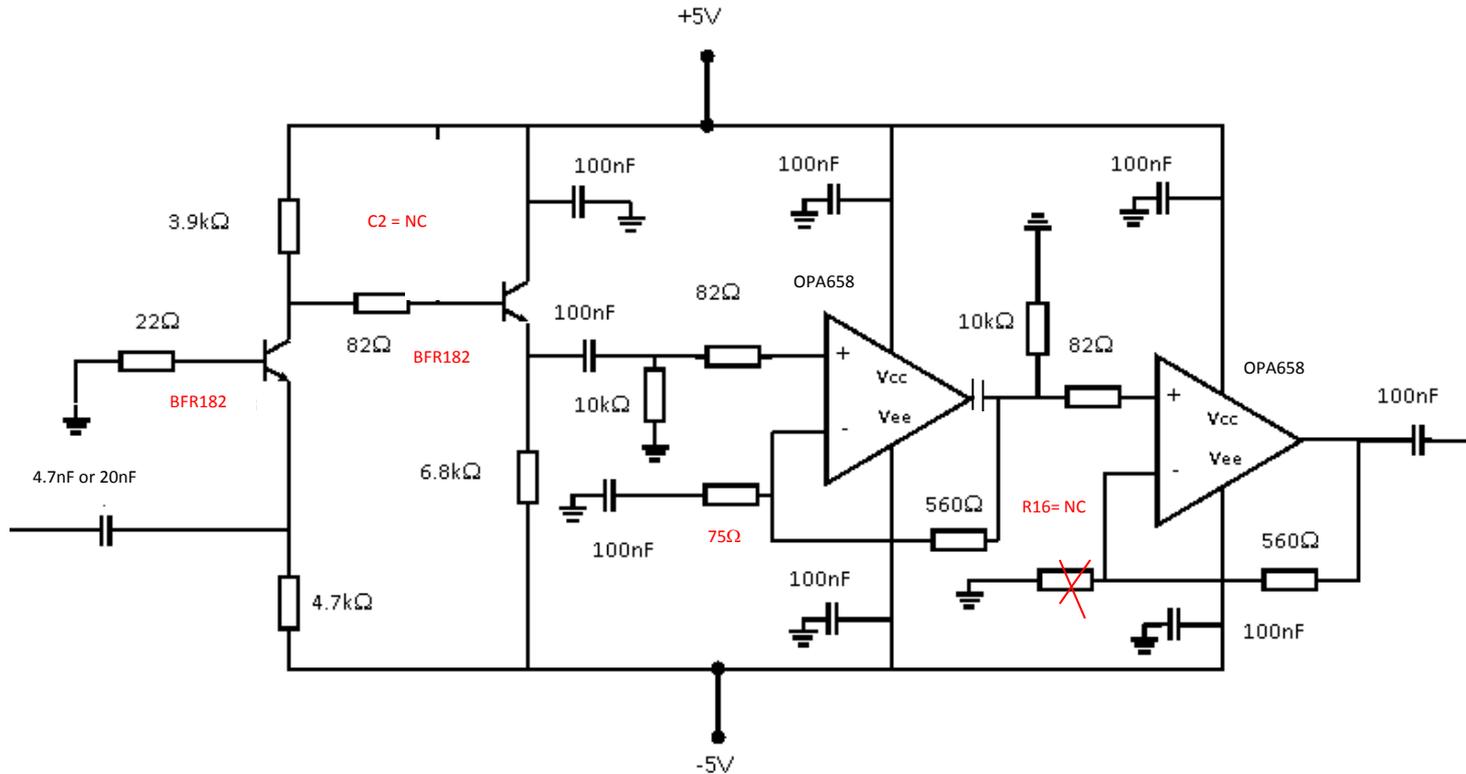Modification of the N055 preamplifier to use $10 \times 10 \text{mm}^2$ APD : sch in red




- C2 = Not connected \Rightarrow bandwidth increase
- Transistor = BFR182 \Rightarrow noise improvement
- Reduction of the gain (factor 4) : $G_{th} = 132878 \text{ V/A} \Rightarrow 33020 \text{ V/A}$

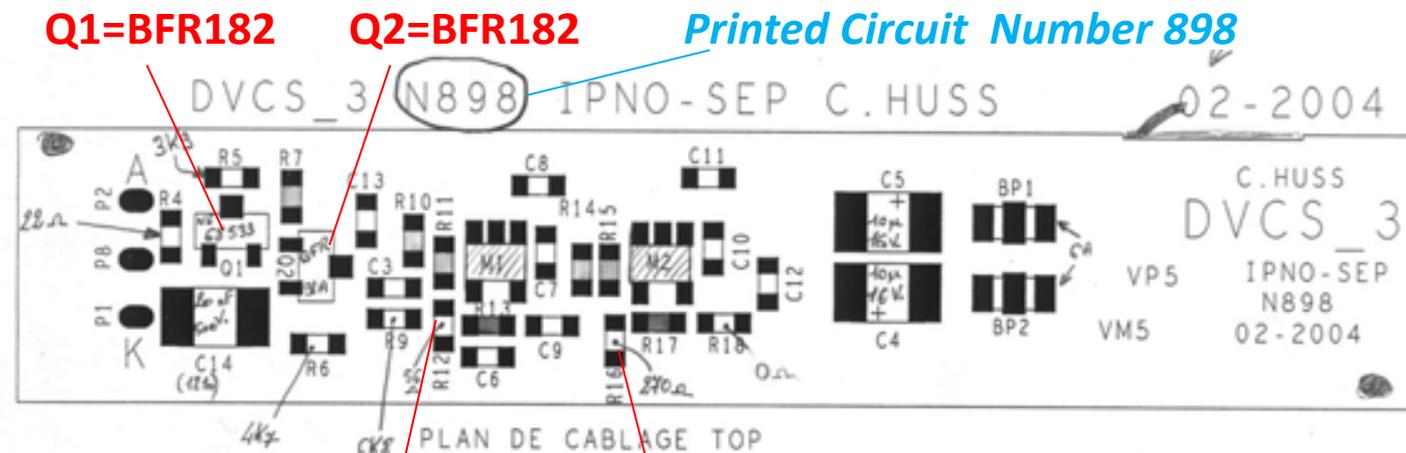Modification of the N055 preamplifier to use $10 \times 10 \text{mm}^2$ APD : **in red**





R12=75Ω

R16=NC

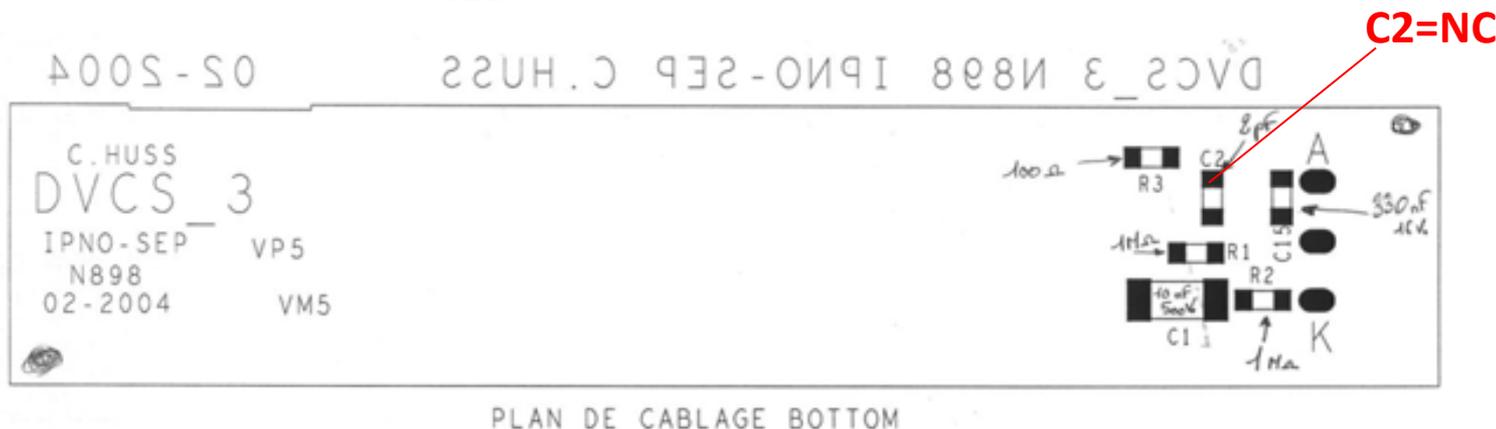

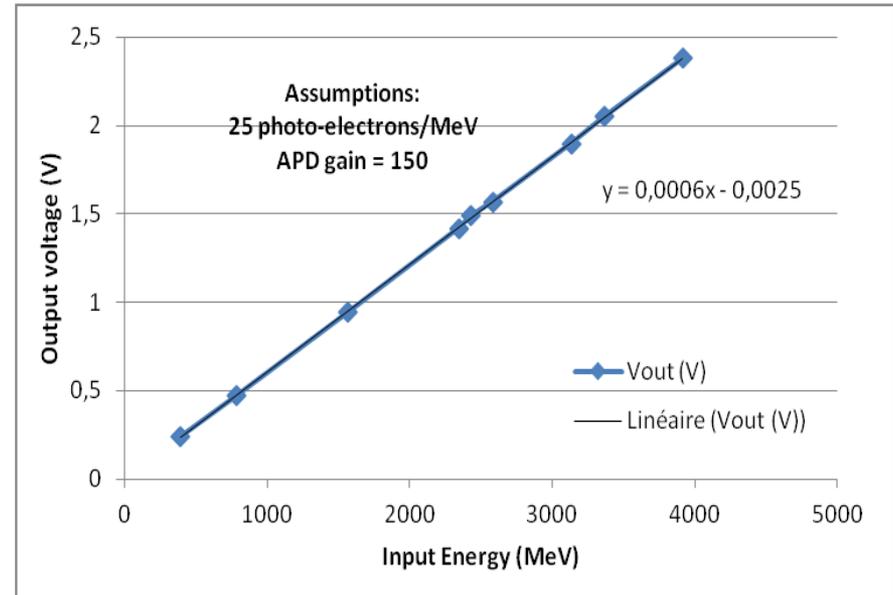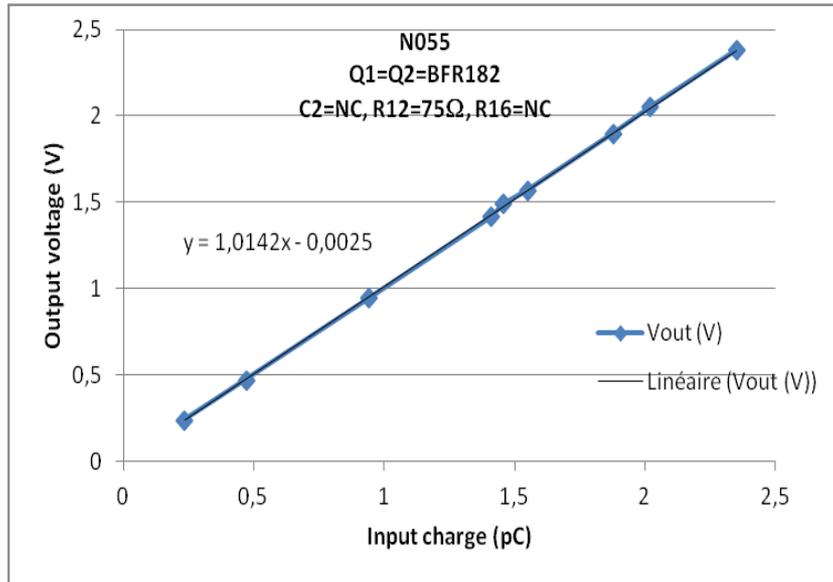Modification of the N055 preamplifier to use $10\times 10\text{mm}^2$ APD : gains



- Gain = **1V/pC** (PW = 20ns) or **0.6mV/MeV** (25 photo-electrons/MeV and APD gain = 150) or **611 pC/pC**(=1.1nC/1.8pC)

Modification of the N055 preamplifier to use $10 \times 10 \text{mm}^2$ APD : signal



- Output signal for $Q_{in}=1.8\text{pC}$ or $E_{in}=3\text{GeV}$ (PW=20ns, 25 photo-electrons/MeV and APD gain =150)
 - ⇒ Gate =75ns down to 65ns
 - ⇒ Amplitude = 1.8V
 - ⇒ Output charge = 1.1nC
 - ⇒ Input noise = 4.2MeV

Conclusion

- With the modified preamplifier, the integration gate could reach 65 ns
- 3GeV corresponds to 1.8V (25 photoelectrons/MeV and APD gain = 150)
- The noise is improved with the modified preamplifier due to new transistors BFR182 (10%) and APD 10×10mm² (90%)

Schedule

- November-december 2013 \Rightarrow the 500 preamplifiers will be sent to IPN-Orsay
- November 2013 \Rightarrow order of 1000 BFR182 and 500 resistances 75Ω with the ANR account
- January-february 2014 \Rightarrow quick test of the 500 preamps to check if they are working

If not, order of new components (OPA658 are obsolete to be replaced by OPA694)

- February-march 2014 \Rightarrow modification of the 500 preamps
- April-may 2014 \Rightarrow detailed tests of the 500 preamps together with a test report
- May 2014 \Rightarrow send back to JLAB